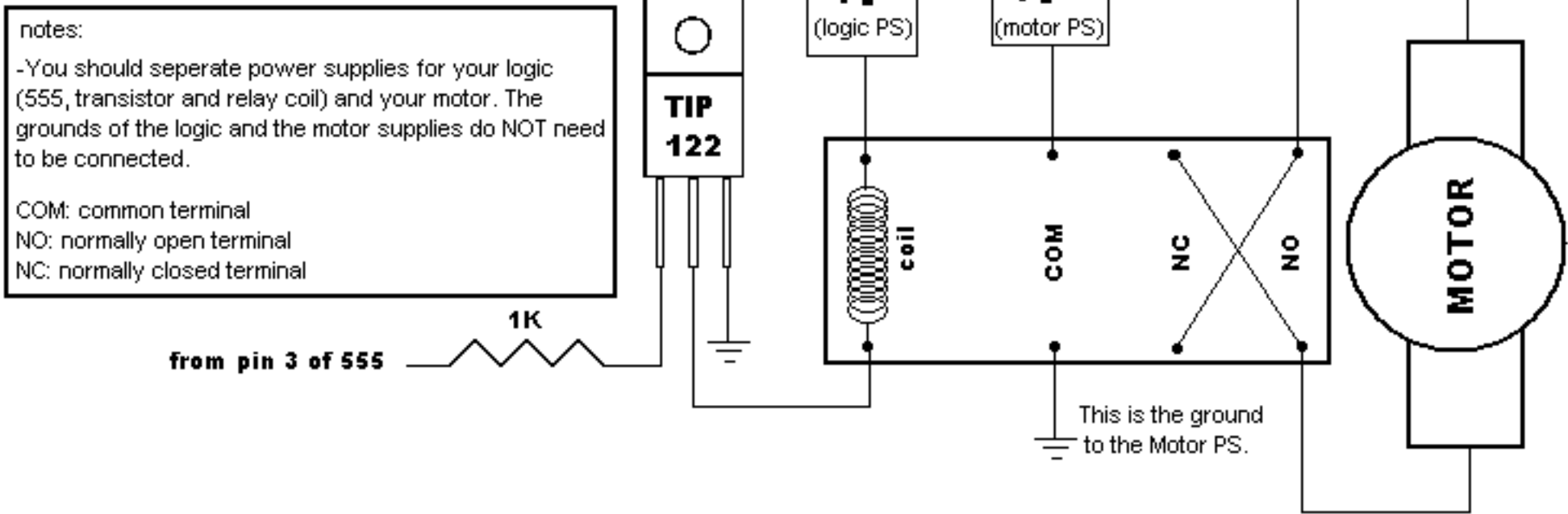


USING A 555 AND A RELAY TO CONTROL MOTOR DIRECTION

PICTORIAL SCHEMATIC:



LOGICAL SCHEMATIC:

